THE MASTERMIND COACHING CLASSES

CBSE / RBSE • NURSERY – CLASS XII • JAIPUR

Road No. 5, VKIA, Jaipur — 9887258679

CLASS 8 — SCIENCE · EASY LEVEL CHAPTER TEST SET 1

Chapter 4: **Electricity: Magnetic and Heating Effects** | RBSE Pattern | Session 2026–27

Time: 1 Hour 30 Minutes Name: _____ Roll No.: _____ **Maximum Marks: 40**

General Instructions:

1. All questions are compulsory.
2. Q. 1–10 are Objective Type (1 mark each).
3. Q. 11–14 are Very Short Answer Type (2 marks each).
4. Q. 15–18 are Short Answer Type (3 marks each).
5. Q. 19–20 are Long Answer Type (5 marks each).
6. Internal choice is given in Q. 17 to 20.
7. Write the question number before each answer.
8. Easy level: direct, single-step questions.

SECTION — A (Objective Type Questions) 10 × 1 = 10

Choose the correct option and write it in your answer book.

1. A cell has: 1

(a) two terminals **(b)** five terminals **(c)** three terminals **(d)** no terminals

2. A circuit with a gap is called: 1

(a) ring circuit **(b)** open circuit **(c)** closed circuit **(d)** short circuit

3. Which of these is a safe practice? 1

(a) overload a socket
(b) use a wet hand on a switch
(c) touch live wires
(d) switch off the supply before fixing a plug

4. The long line in the cell symbol is: 1

(a) positive terminal **(b)** bulb
(c) switch **(d)** negative terminal

5. A complete circuit is called a: 1

(a) broken circuit **(b)** wrong circuit **(c)** closed circuit **(d)** open circuit

6. A wire heated by current becomes: 1

(a) cold **(b)** magnetic only **(c)** hot **(d)** wet

7. A good conductor is: 1

(a) plastic **(b)** wood **(c)** copper **(d)** glass

8. An electric cell changes: 1

(a) light into sound **(b)** chemical energy into electrical energy
(c) heat into chemical **(d)** sound into heat

9. Electric crane in a junkyard uses: 1

(a) an electromagnet **(b)** a bulb **(c)** a cell only **(d)** a compass

10. An insulator is: 1

(a) rubber **(b)** silver **(c)** copper **(d)** iron

SECTION — B (Very Short Answer Type) 4 × 2 = 8

Answer in about 20–30 words each.

11. Name the parts of a simple electric circuit. 2

12. What is a fuse? 2

13. What is a short circuit? 2

14. Name two conductors. 2

SECTION — C (Short Answer Type) — 4 × 3 = 12

Answer in about 40–60 words each.

15. Draw in words a circuit with a bulb and a cell. 3

16. Write three safety rules for electricity. 3

17. Why do we use thin nichrome wire in heaters? 3

OR

List three conductors and three insulators. 3

18. What are the causes of fire in a house wiring? 3

OR

State three differences between a fuse and an MCB. 3

SECTION — D (Long Answer Type) — 2 × 5 = 10

Answer in about 100–150 words each.

19. Describe how a simple electric circuit works and its parts. 5

OR

Write about the working of an electric bell. 5

20. Describe how to test conducting and insulating materials. 5

OR

List five safety rules with reasons. 5

END OF QUESTION PAPER — Total: 40 Marks

MASTERMIND