THE MASTERMIND COACHING CLASSES

CBSE / RBSE • NURSERY – CLASS XII • JAIPUR

Road No. 5, VKIA, Jaipur — 9887258679

CLASS 7 — SCIENCE · EASY LEVEL CHAPTER TEST SET 2

Chapter 2: **Electricity: Circuits and their Components** | RBSE Pattern | Session 2026–27

Time: 1 Hour 30 Minutes Name: _____ Roll No.: _____ **Maximum Marks: 40**

General Instructions:

1. All questions are compulsory.
2. Q. 1–10 are Objective Type (1 mark each).
3. Q. 11–14 are Very Short Answer Type (2 marks each).
4. Q. 15–18 are Short Answer Type (3 marks each).
5. Q. 19–20 are Long Answer Type (5 marks each).
6. Internal choice is given in Q. 17 to 20.
7. Write the question number before each answer.
8. Easy level: direct, single-step questions.

SECTION — A (Objective Type Questions) 10 × 1 = 10

Choose the correct option and write it in your answer book.

1. Wet hands touching a switch can cause: 1

(a) cold **(b)** shock **(c)** light **(d)** sound

2. A switch in the off position makes the circuit: 1

(a) short **(b)** parallel **(c)** open **(d)** closed

3. In an open circuit current: 1

(a) reverses **(b)** doubles **(c)** flows **(d)** does not flow

4. An electric heater works on the: 1

(a) magnetic effect **(b)** heating effect of current
(c) light effect **(d)** sound effect

5. Electricity must be used: 1

(a) carefully **(b)** carelessly
(c) with wet hands **(d)** with damaged wires

6. In a closed circuit current: 1

(a) breaks **(b)** stops **(c)** does not flow **(d)** flows

7. An electric iron works on: 1

(a) heating effect of current **(b)** sound
(c) chemical effect **(d)** light

8. We should switch off appliances when: 1

(a) never **(b)** in use **(c)** not in use **(d)** always

9. A conductor is a material that: 1

(a) stops electricity **(b)** allows electricity to pass
(c) makes electricity **(d)** breaks wires

10. Electric current flows from: 1

(a) the wire to the table **(b)** the switch to the sky
(c) the bulb to the air **(d)** the cell through the circuit

SECTION — B (Very Short Answer Type) 4 × 2 = 8

Answer in about 20–30 words each.

11. Name two insulators. 2

12. What is a closed circuit? 2

13. What is a circuit? 2

14. What is a filament? 2

SECTION — C (Short Answer Type) — 4 × 3 = 12

Answer in about 40–60 words each.

15. Name three insulators. 3

16. Why does a bulb not glow in an open circuit? 3

17. Write three things that do not conduct electricity. 3

OR

Write three electrical safety rules. 3

18. Why is a fuse needed in a house? 3

OR

Why is a thick wire used for heavy appliances? 3

SECTION — D (Long Answer Type) — 2 × 5 = 10

Answer in about 100–150 words each.

19. Write five safety rules for electricity. 5

OR

Write about LED and ordinary bulbs in five points. 5

20. Explain the working of an electric iron. 5

OR

Explain how to make a battery with three cells. 5

END OF QUESTION PAPER — Total: 40 Marks

MASTERMIND