THE MASTERMIND COACHING CLASSES

CBSE / RBSE • NURSERY – CLASS XII • JAIPUR

Road No. 5, VKIA, Jaipur — 9887258679

CLASS 7 — SCIENCE · EASY LEVEL CHAPTER TEST SET 1

Chapter 2: **Electricity: Circuits and their Components** | RBSE Pattern | Session 2026–27

Time: 1 Hour 30 Minutes Name: _____ Roll No.: _____ **Maximum Marks: 40**

General Instructions:

1. All questions are compulsory.
2. Q. 1–10 are Objective Type (1 mark each).
3. Q. 11–14 are Very Short Answer Type (2 marks each).
4. Q. 15–18 are Short Answer Type (3 marks each).
5. Q. 19–20 are Long Answer Type (5 marks each).
6. Internal choice is given in Q. 17 to 20.
7. Write the question number before each answer.
8. Easy level: direct, single-step questions.

SECTION — A (Objective Type Questions) 10 × 1 = 10

Choose the correct option and write it in your answer book.

1. A cell is a source of: 1

(a) electricity **(b)** water **(c)** air **(d)** oil

2. Electric wires are made of: 1

(a) wood **(b)** plastic **(c)** rubber **(d)** copper

3. The positive terminal of a cell is the: 1

(a) cap **(b)** bulb **(c)** flat base **(d)** wire

4. A battery has: 1

(a) one switch **(b)** one bulb

(c) two or more cells **(d)** no cells

5. Wires are covered with: 1

(a) paper **(b)** cotton **(c)** copper **(d)** plastic

6. The negative terminal of a cell is the: 1

(a) cap **(b)** switch **(c)** bulb **(d)** flat base

7. A bulb has a: 1

(a) filament **(b)** cell **(c)** fuse **(d)** fan

8. A fuse is used for: 1

(a) safety **(b)** decoration **(c)** light **(d)** sound

9. A circuit diagram shows: 1

(a) a poster **(b)** a map

(c) a photo **(d)** connections using symbols

10. A switch is used to: 1

(a) open or close a circuit **(b)** store current

(c) make electricity **(d)** make light

SECTION — B (Very Short Answer Type) 4 × 2 = 8

Answer in about 20–30 words each.

11. What is a cell? 2

12. Name two conductors. 2

13. What is an open circuit? 2

14. What is a battery? 2

SECTION — C (Short Answer Type) 4 × 3 = 12

Answer in about 40–60 words each.

15. Name three parts of a simple circuit. 3

16. Write the symbols of a cell, a bulb and a switch (describe). 3

17. Why do we use switches? 3

OR

Name three conductors. 3

18. How do you make a bulb glow? 3

OR

Write three things that conduct electricity. 3

SECTION — D (Long Answer Type) 2 × 5 = 10

Answer in about 100–150 words each.

19. Describe how to light a bulb with a cell and wires. 5

OR

Write five uses of electric current. 5

20. Write three conductors and two insulators. 5

OR

Describe why a fuse blows. 5

END OF QUESTION PAPER Total: 40 Marks

MASTERMIND